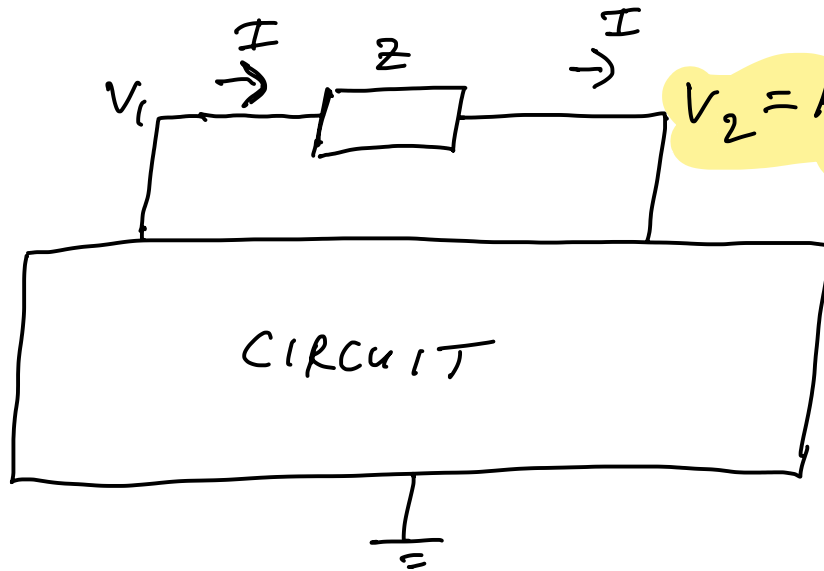


MILLER'S THEOREM

- ⇒ "MILLER EFFECT" DESCRIBED BY JOHN MILLER IN 1920
- ⇒ FORMALIZED IN 1972 AS "MILLER'S THEOREM"
- ⇒ USED TO CHANGE A SINGLE IMPEDANCE BETWEEN 2 NODES INTO 2 GROUNDED IMPEDANCES
- ⇒ A COMMON EXAMPLE IS C_{gd} IN A TRANSISTOR AND WANT TO FIND C_g CAPACITANCE TO GROUND

MILLER'S THEOREM



⇒ USED TO BREAK UP A COUPLING IMPEDANCE BETWEEN 2 NODES



$$V_2 = kV_1$$

$$I = \frac{V_1 - V_2}{Z}$$

$$I = \frac{V_1 - kV_1}{Z}$$

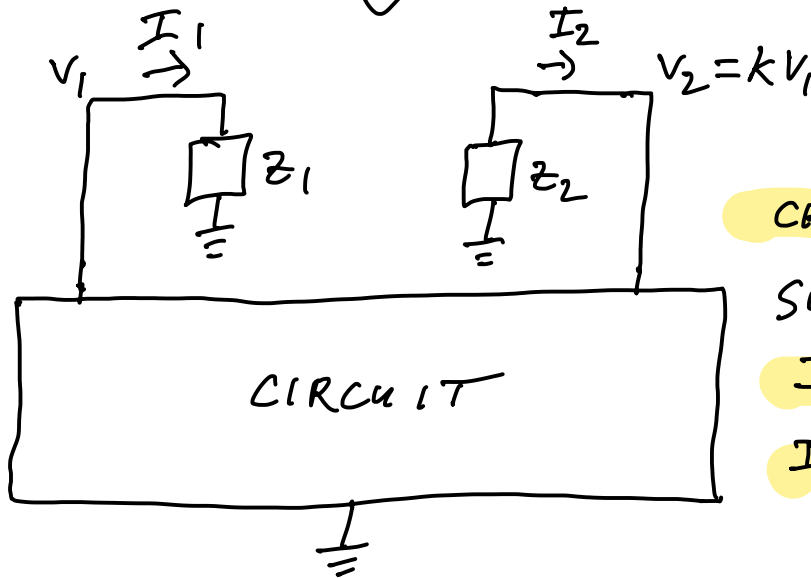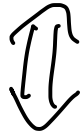

CHOOSE Z_1 + Z_2

SUCH THAT

$$I_1 = I$$

$$I_2 = I$$

$$Z_1 = \frac{Z}{1-k}$$

$$Z_2 = \frac{Z}{(1 - \frac{1}{k})}$$

PROOF

$$I = \frac{V_1 - kV_1}{Z} \quad I_1 = \frac{V_1}{Z_1}$$

$$\text{FOR } I_1 = I \Rightarrow \frac{V_1}{Z_1} = \frac{V_1 - kV_1}{Z}$$

$$\Rightarrow Z_1 = \frac{Z}{1-k}$$

$$\text{ALSO } I_2 = \frac{0 - V_2}{Z_2} = \frac{0 - kV_1}{Z_2}$$

$$\text{FOR } I_2 = I \Rightarrow \frac{-kV_1}{Z_2} = \frac{V_1 - kV_1}{Z}$$

$$\Rightarrow Z_2 = \frac{Z}{(1 - \frac{1}{k})}$$

$$\text{IF } Z = R \Rightarrow R_1 = \frac{R}{1-k}$$



$$R_2 = \frac{R}{(1 - \frac{1}{k})}$$

$$\text{IF } Z = \frac{1}{sC} \Rightarrow C_1 = C(1-k)$$

$$C_2 = C(1 - \frac{1}{k})$$

MT3

EX

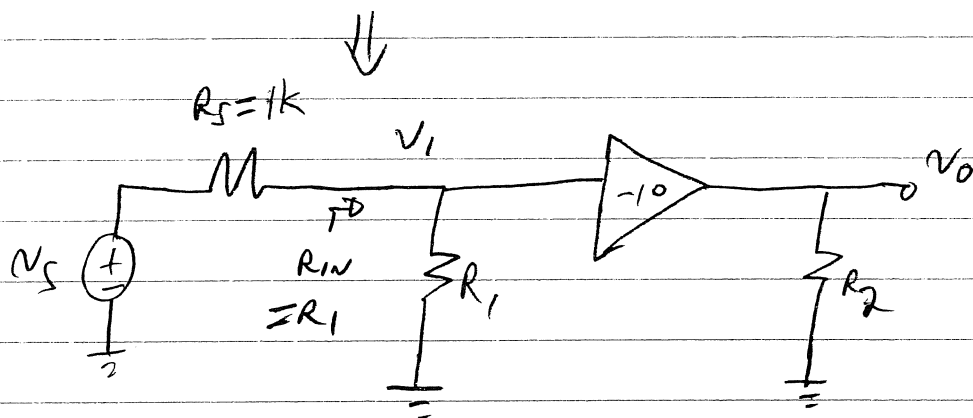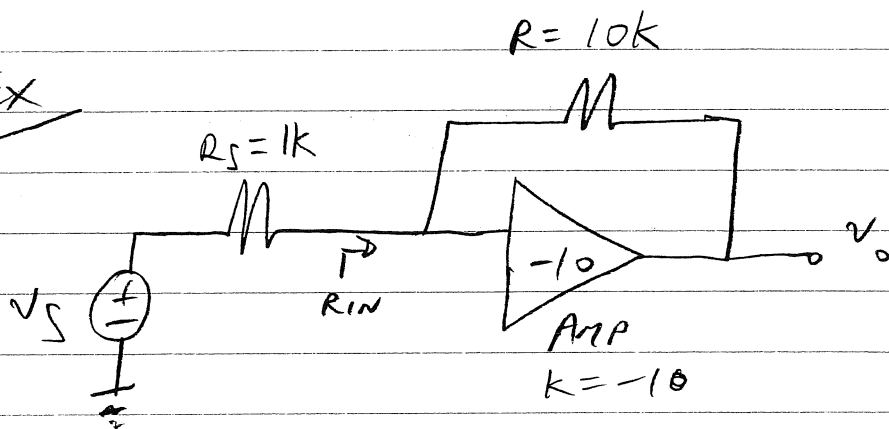

$$R_1 = \frac{R}{1-k} = \frac{10k}{1-(-10)} = \frac{10k}{11} = 909.1 \Omega$$

$$V_1 = \frac{R_1}{R_1 + R_S} V_S = 0.476 V_S$$


$$V_O = -10 V_1 = -4.76 V_S$$

$$R_2 = \frac{R}{1 - 1/k} = \frac{10k}{1 + (1/10)} = 9.1k \approx R$$

NOT
MUCH
CHANGE

MT4


EX

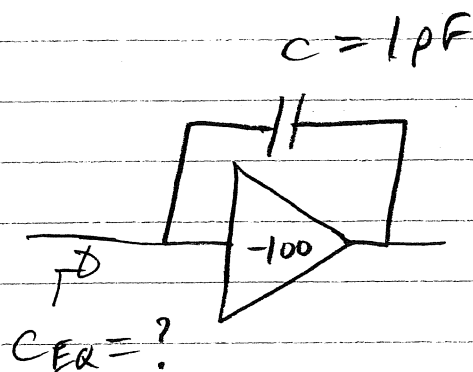

$$C_{EQ} = C(1 + 100) = 101C = 101 \text{ pF}$$

EX

BOOT STRAPPING

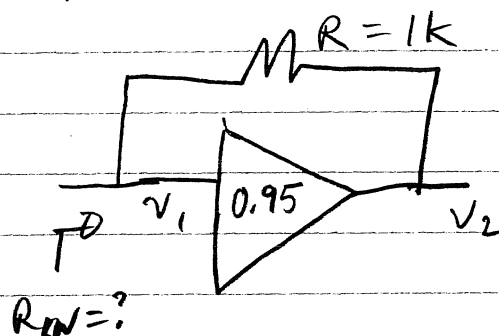


$$R_{in} = \frac{R}{1 - 0.95} = \frac{R}{0.05} = 20R = 20 \text{ k}\Omega$$

SINCE $V_2 \approx V_1$ LITTLE CURRENT
FLOWS THROUGH R AND IMPEDANCE
INCREASED

EX

BOOTSTRAPPING WITH A CAPACITOR

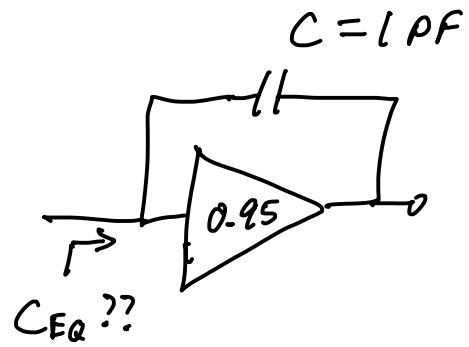

$$C_{EQ} = C(1 - 0.95) = C(0.05) = 50 \text{ fF}$$